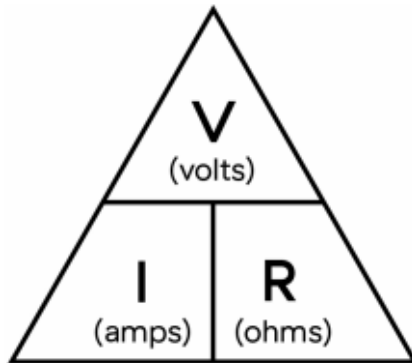


# Ohm's Law

Ms. McDade

The relationship between voltage, current and resistance is shown in this graphic:




$$V = I \times R$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

- 1) A smartphone with a resistance of 35 ohms has a current of 0.25 amps flowing through it. Calculate how many volts supply the smart phone.
  
  
  
  
  
  
  
  
  
  
- 2) A 120-volt power source supplies a computer with a resistance of 210 ohms. What is the current flow of the circuit?

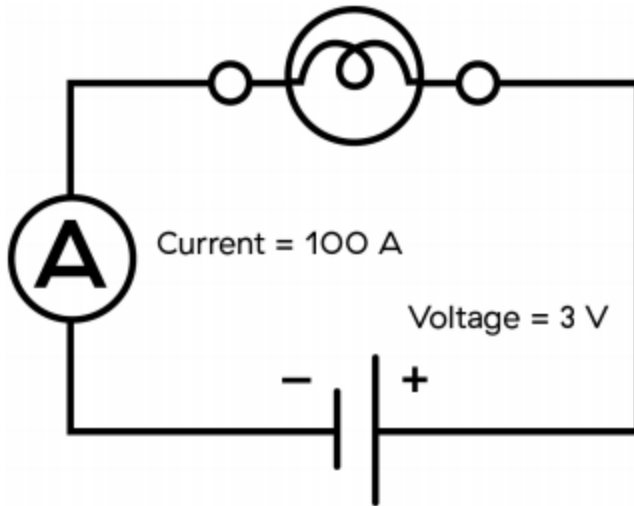3) Calculate the resistance of the following circuit diagram:



4) What amount of voltage would you need to run a current of 1.2 amps through a 250-ohm resistor?

5) Using the given variables, calculate the unknown value:

a)  $V = 10 \text{ V}$      $R = 5 \Omega$      $I = \underline{\hspace{2cm}} \text{ A}$

b)  $V = 3.5 \text{ V}$      $R = 10 \Omega$      $I = \underline{\hspace{2cm}} \text{ A}$

c)  $V = 10 \text{ V}$      $I = 2 \text{ A}$      $R = \underline{\hspace{2cm}} \Omega$

d)  $V = 3.5 \text{ V}$      $I = 0.5 \text{ A}$      $R = \underline{\hspace{2cm}} \Omega$

e)  $I = 11 \text{ A}$      $R = 3 \Omega$      $V = \underline{\hspace{2cm}} \text{ V}$

f)  $I = 7 \text{ A}$      $R = 4.5 \Omega$      $V = \underline{\hspace{2cm}} \text{ V}$